
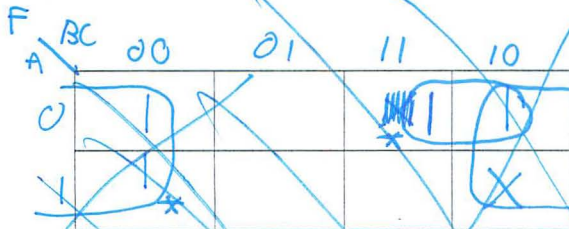


CE-1901-11 - Dr. Durant - Quiz 5
Fall 2016, Week 5 Quiz

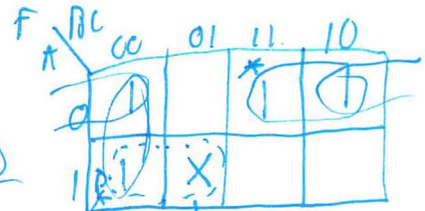1. (1.5 points) Let $F(ABC) = \sum_m(0, 2, 4) + d(3, 4)$ (d indicates don't care conditions). Derive the simplest SOP expression for F using a K-map. **Reminders:** adjacent terms in a K-map may differ in the value of only 1 bit. Start with m_0 in the upper left corner, putting m_1 to the right and m_4 below it. Form largest groups possible. It is okay to cover terms more than once as your form larger implicants.





$$F = \bar{C} + \bar{A}B$$






$$F = \bar{B}\bar{C} + \bar{A}B$$

can mark, but clearly not needed, so can do it

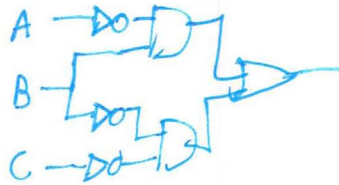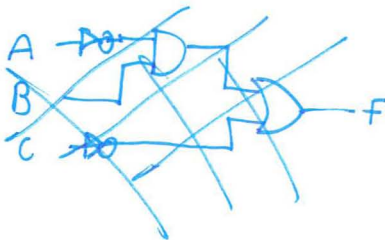2. (1 point) Draw your reduced circuit for F directly using NOT-AND-OR gates.



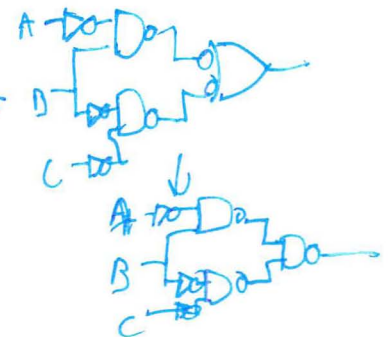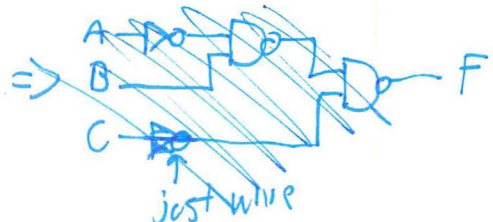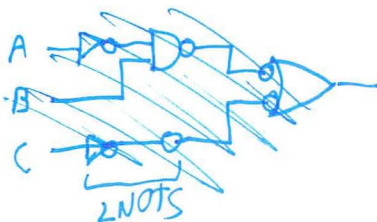3. (2 points) Re-draw it using just NAND and NOT gates based on the most simplified SOP form. **Reminders:** The first step is to put 2 NOT gates on every input to the OR gate. After that, apply DeMorgan's Theorems (bubble pushing).



4. (1 point) Calculate the number of transistors needed for each reduced implementation above.

#2: 2	NOT	4T
1	AND2	6T
1	OR2	6T
		<u>16</u>

#3: 1	NOT	4T
2	NAND2	8T
		<u>12T</u>

#2: 3	NOT: 6
2	AND2: 12
1	OR2: 6
	<u>24</u>


#3: 3	NOT: 6
2	AND2: 12
	<u>18</u>

Let $H(ABCD) = \Sigma_m(2, 3, 4, 6, 7, 10, 11, 12, 14, 15)$. Derive the simplest SOP expression for H using a K-map. $H = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$



- (b) Draw truth map that results in the K-Map equation: $\bar{x} + y$
-
- The Karnaugh map for the equation $\bar{x} + y$ is shown below. The map is a 2x4 grid with columns labeled 00, 01, 11, 10 and rows labeled 0, 1. The top row (y=0) has a 1 in the 10 column, which is circled and labeled $\bar{x} + y$. The bottom row (y=1) has a 1 in the 00 column, which is circled and labeled $\bar{x} + y$. The final expression $\bar{x} + y$ is written at the bottom right.

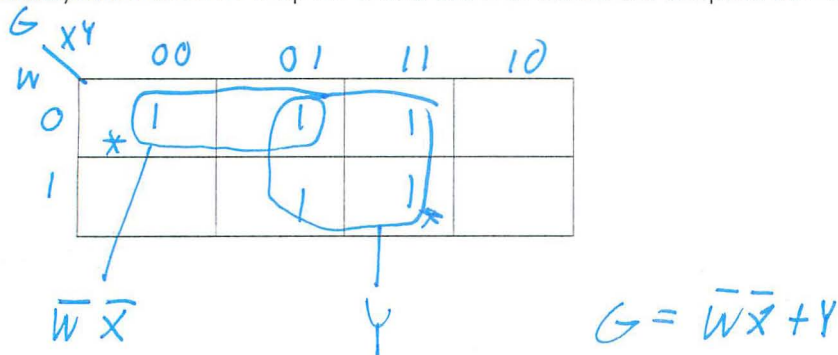
7. (2 points) ^{1.5}**Draw** another map for G and use it to **derive** the simplest SOP expression for G.



Note: this is also an application of the distributive theorem.


CE-1901-12 - Dr. Durant - Quiz 5
Fall 2016, Week 5 Quiz

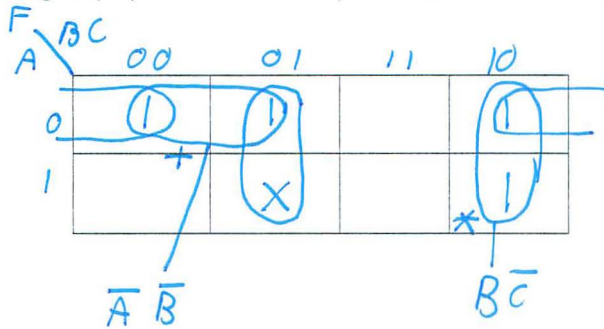1. (1.5 points) Let $F(ABC) = \Sigma_m(0, 1, 2, 6) + d(5)$ (d indicates don't care conditions). Derive the simplest SOP expression for F using a K-map. **Reminders:** adjacent terms in a K-map may differ in the value of only 1 bit. Start with m_0 in the upper left corner, putting m_1 to the right and m_4 below it. Form largest groups possible. It is okay to cover terms more than once as your form larger implicants.




$$F = \bar{A}\bar{B} + B\bar{C}$$

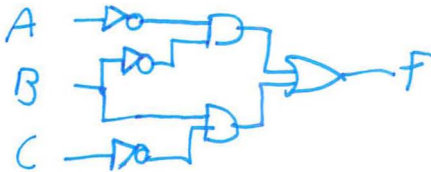2. (1 point) Draw your reduced circuit for F directly using NOT-AND-OR gates.



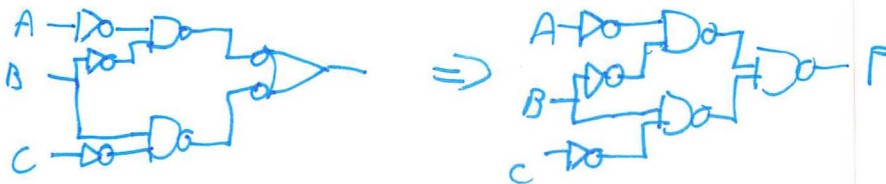3. (1 point) Re-draw it using just NAND and NOT gates based on the most simplified SOP form. **Reminders:** The first step is to put 2 NOT gates on every input to the OR gate. After that, apply DeMorgan's Theorems (bubble pushing).




4. (1 point) Calculate the number of transistors needed for each reduced implementation above.

$$\begin{array}{lcl} \#2: & 3 \text{ NOT} & 6T \\ & 2 \text{ AND2} & 12T \\ & 1 \text{ OR2} & 6T \\ & \hline & & 24T \end{array}$$

$$\begin{array}{lcl} \#3: & 3 \text{ NOT} & = 6T \\ & 3 \text{ NAND2} & = 12T \\ & \hline & & 18T \end{array}$$

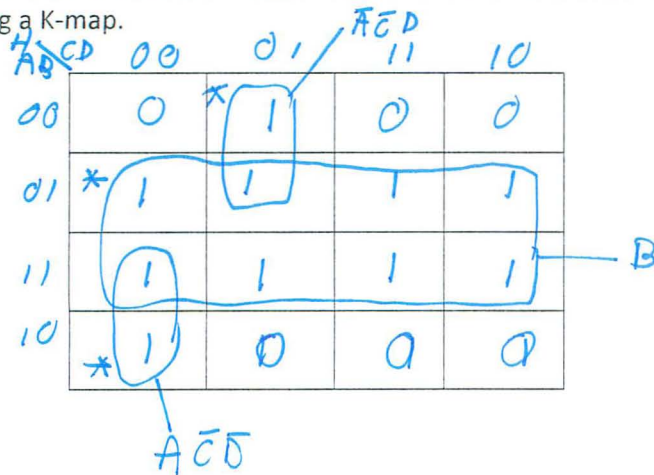5. (2 points) Let $H(ABCD) = \sum_m(1, 4, 5, 6, 7, 8, 12, 13, 14, 15)$. Derive the simplest SOP expression for H using a K-map.




$$F = B + \bar{A}\bar{C}D + A\bar{C}\bar{D} \leftarrow \text{ANSWER}$$


$$= B + \bar{C}(\bar{A}D + A\bar{D})$$

$$= B + \bar{C}(A \oplus D) \leftarrow \text{No longer SOP}$$

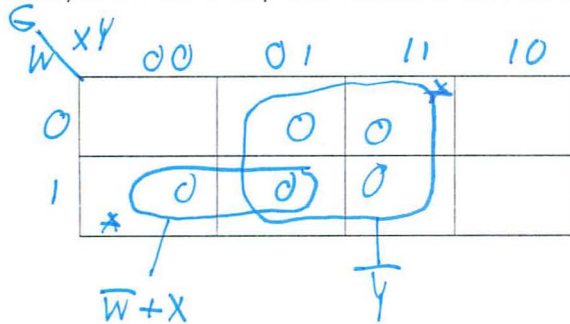6. (2 points) **Draw** the K-map that results in the POS equation $G(WXY) = (Y')(W'+X)$.



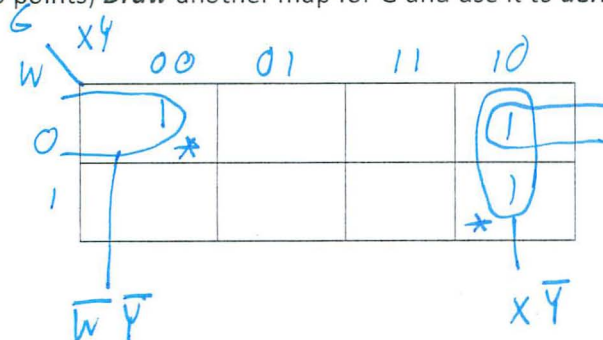7. (1.5 points) **Draw** another map for G and use it to **derive** the simplest SOP expression for G.



$$G = \bar{W}\bar{Y} + X\bar{Y} \leftarrow \text{answer}$$

$= \bar{Y}(\bar{W}+X)$ Boolean algebra, distributive theorem, another way to move back to POS, in this case